

# STUDY OF LATTICE VIBRATIONS USING ELECTRONIC CIRCUITS

NAME - ARYAN SHRIVASTAVA

ROLL NO. - 231104)

DATE OF EXPERIMENT - 28/01/26 & 29/01/26

DATE OF SUBMISSION - 04/02/26

## Abstract

In this experiment, LC circuits were used as analogues of monoatomic and diatomic lattices to study lattice vibrations & their dispersion relations. The frequency was plotted against phase per unit cell & a cut-off frequency was observed for monoatomic case. For diatomic lattice, two branches corresponding to acoustic & optical modes were observed & frequency band gap was calculated. The results confirm the validity of electrical analogue model for studying lattice vibrations.

## # Objective :-

- i) Build an analogy of mono-atomic lattice using inductors & capacitors & study dispersion relation.
- ii) Build an analogy of di-atomic lattice using inductors & two different capacitors & study dispersion relation & band-gap energy.

## # Theory :-

Consider a spring-mass model of a periodic mono-atomic lattice in one-direction. Atoms having mass 'm' connected by a force constant 'f'. (See fig.)

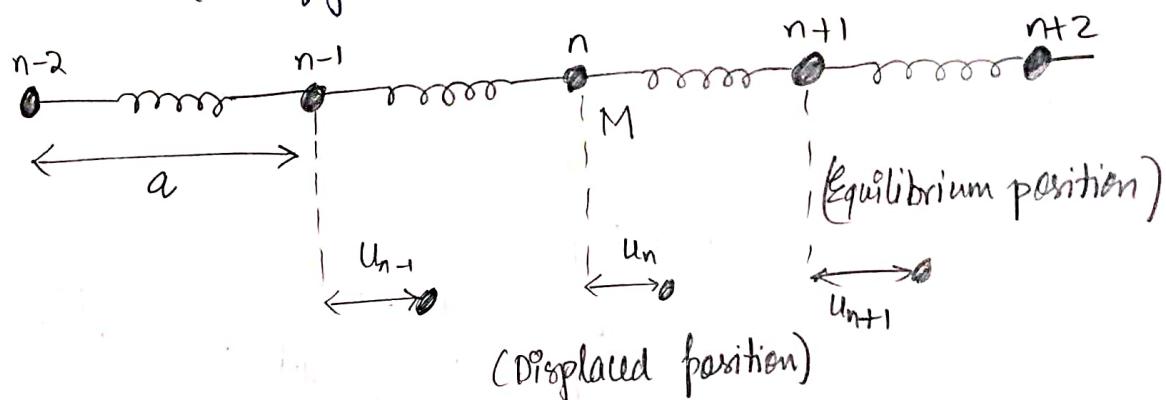


Figure:- 1D linear Monoatomic lattice with  
 $a \rightarrow$  Lattice constant  
 $f \rightarrow$  force constant  
 $M \rightarrow$  Mass of the atom

The array is assumed to be infinitely long. Assuming only the nearest neighbour interaction, the equation of motion of  $n^{\text{th}}$  atom is given by:

$$\ddot{u}_n = f((u_{n+1} + u_{n-1}) - 2u_n) \quad \text{--- (I)}$$

Attempting solution to (I) of the form,

$$u_n = A e^{i(k_n a - \omega t)} \quad A e^{i(nk a - \omega t)}$$

$$\ddot{u}_n = -\omega^2 u_n = \frac{f}{m} ((u_{n+1} + u_{n-1}) - 2u_n)$$

$$u_k(n, t) = A e^{i(nk a - \omega t)} \quad u_{k \cdot (n \pm 1, t)} = A e^{i((k \pm 1)ka - \omega t)}$$

$$-\omega^2 e^{inka} = \frac{f}{m} (e^{i(n+1)ka} + e^{i(n-1)ka} - 2e^{inka})$$

$$-\omega^2 = \frac{f}{m} (e^{ika} + e^{-ika} - 2) = 2\frac{f}{m} (\cos ka - 1)$$

$$\Rightarrow \omega^2 = \frac{2f}{m} (1 - \cos ka) \Rightarrow \underline{\omega = \sqrt{\frac{4f}{m}} \left| \sin\left(\frac{ka}{2}\right) \right|}$$

$$\boxed{\omega^2 = \frac{2f}{m} (1 - \cos\theta)}$$

where  $k$  = wave vector =  $\frac{2\pi}{\lambda} = \frac{\omega}{c}$

$c$  = velocity of propagation

$\theta = ka$  = phase change per unit cell

$$\boxed{\nu_{\max} = \frac{\omega_{\max}}{2\pi} = \frac{1}{\pi} \sqrt{\frac{f}{m}}}$$

Beyond this frequency, no transmission occurs. This is analogous to a low-pass filter circuit which transmits in the range  $0 - \nu_{\max}$ . (see fig.)

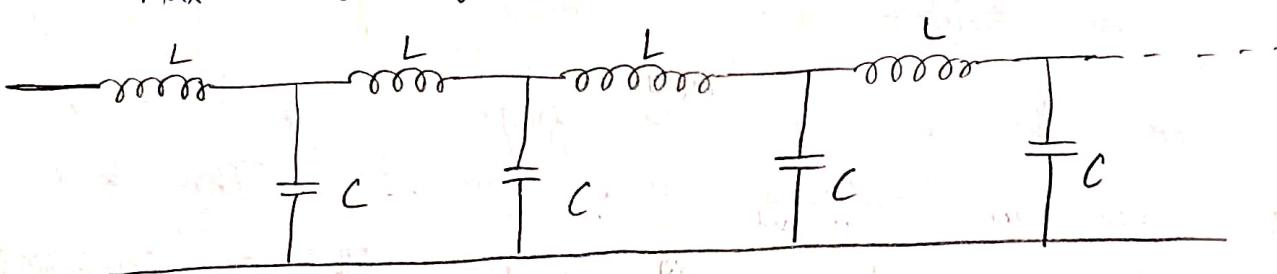


Figure 2 : Electrical Analogue of linear-mono-atomic lattice  
(Low-pass filter)

The dispersion relation for this circuit is

$$\boxed{\omega^2 = \frac{2}{LC} (1 - \cos\theta)}$$

where  $\theta$  = phase change due to 1 section (unit cell) of the filter.

~~For 2nd year~~ Analog :  $(L) \leftrightarrow \frac{mf}{\omega}$  &  $(\frac{1}{C}) \leftrightarrow \frac{f}{m}$ . Studying the phase difference b/w input & output voltages of the circuit as a function of frequency, the dispersion relation may be verified.

## \* Di-atomic Lattice.

Consider a di-atomic lattice with alternative masses 'm' & 'M' as shown in fig. It can be simulated by a transmission line with alternative capacitors 'C' & 'G' as shown in figure.

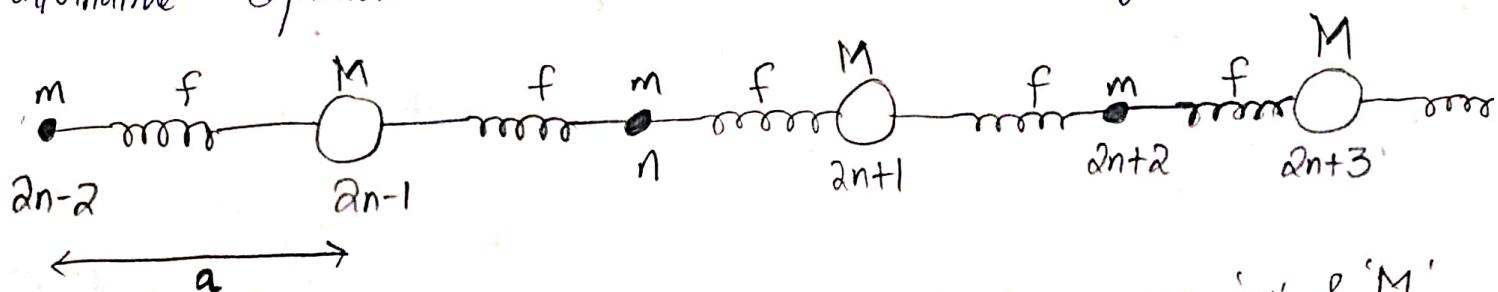


Figure :- Linear - Di-atomic lattice of lattice constant 'a', masses 'm' & 'M' and force constant 'f'

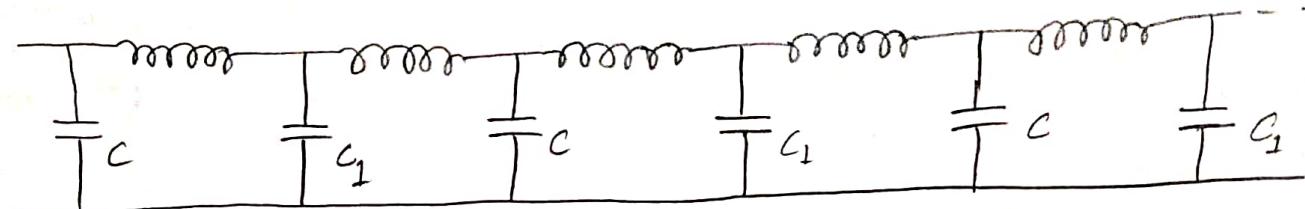


Figure :- Linear diatomic lattice -- electrical analogue.

In this case, there are now two frequencies  $\omega_+$  &  $\omega_-$ , corresponding to a particular wave vector 'k'. This leads to two branches in the  $\omega$  vs  $k$  plot. The one corresponding to  $\omega_+$  is called optical branch & the one for  $\omega_-$  is called acoustical branch. The frequency gap between these branches depends on  $(\frac{M}{m}) \leftrightarrow (\frac{C}{G})$ .

## # Apparatus required :-

- i) Function generator (signal generator)
- ii) Oscilloscope
- iii) Breadboard
- iv) connecting wires & BNC cables.
- v) Inductors
- vi) capacitors (2 types)

# atomic lattice:-

# Monatomic (small mass/capacitance) N = 10

Capacitance  
(C)  $\text{nF}$

frequency f (kHz)	Phase difference (degrees)	Lissajous figure	frequency per unit cell (kHz)	<del>C (nF)</del>	$C_1 (\text{nF})$
0.025	0°	/	0°	149.68	49.01
3.25	90°	○	9°		47.12
7.00	180°	/	18°		47.71
10.65	270°	○	27°		47.38
14.35	360°	/	36°		49.50
17.70	450°	○	45°		47.93
21.30	540°	/	54°		48.05
24.65	630°	○	63°		49.81
27.95	720°	/	72°		45.88
31.00	810°	○	81°		
34.0	900°	/	90°		
36.5	990°	○	99°		
39.0	1080°	/	108°		
41.5	1170°	○	117.8°		
43.5	1255°	/	125.5°		
45.5	1340°	○	134°		
<del>Scal 1/25</del>				$C_{avg} = 48.02 \text{ nF}$	

$$V_{max} = \frac{1}{\pi} \sqrt{\frac{1}{LC}}$$

$$= \frac{1}{\pi} \sqrt{\frac{10^{-12}}{0.974 \times 48.02}}$$

$$V_{max} = 46.54 \text{ kHz}$$

# Observations :-  $\epsilon = 150.42 \text{ nF}$  (phase diff) Measurements :-  $N=10$  Obs

Frequency (kHz)	Phase difference (degree)	Lissajous figure	Frequency per unit cell	Inductance (L) (mH)	Capacitance (C) (nF)
1. 0.025	0	/	0	0.968	144.59
2. 1.695	90°	O	9	0.982	149.65
3. 3.80	180°	/	180°	0.973	144.24
4. 5.75	270°	O	27°	0.964	150.19
5. 7.90	360°	/	36°	0.980	153.67
6. 9.85	450°	O	45°	0.981	155.49
7. 11.80	540°	/	54°	0.972	147.63
8. 13.70	630°	O	63°	0.974	149.38
9. 15.655	720°	/	$\omega_{\max} = \frac{1}{\pi} \sqrt{\frac{1}{LC}}$	$\omega_{\max} = \frac{1}{\pi} \sqrt{\frac{1}{0.974 \times 10^{-3} \times 149.28 \times 10^{-9}}}$	$C_{avg} = 149.28 \text{ nF}$
10. 17.30	810°	O	$\omega_1 = \frac{1}{\pi} \sqrt{\frac{1}{LC}}$	$\omega_{\max} = 0.0264 \times 10^6 \text{ Hz}$	
11. 19.00	900°	/	$\omega_{\max} = 0.0264 \times 10^6 \text{ Hz}$		
12. 20.60	990°	O	$\omega_{\max} = 26.4 \text{ kHz}$		
13. 22.10	1080°	/			
14. 23.45	1170°	O			
15. 24.75	1260°	/			
16. 25.90	1350°	O			
17. 27.05	1440°	/			

(Monatomic lattice)

Ramya

Observation :-

N = 5

(Diatomic lattice)

	Frequency $f$ (kHz)	Phase $\theta$ (deg.)	Lissajous figure	Frequency Phase per unit cell (kHz). different
1.	0.025	0°	/	0
2.	2.075	90°	/	18°
3.	4.505	180°	/	18° 36°
4.	6.95	270°	/	27° 54°
5.	9.25	360°	/	72°
6.	11.55	450°	/	90°
7.	13.75	540°	/	108°
8.	15.70	630°	/	126°
9.	17.65	720°	/	144°
10.	19.55	810°	/	162°
11.	33.5	900°	/	198°
12.	35.0	1080°	/	216°
13.	36.0	1160°	/	232°
14.	37.0	1240°	/	248°
15.	38.5	1370°	/	274°
16.	39.5	1450°	/	290°

## Diatomic Lattice.

C	G
149.72	47.83
151.23	48.04
150.99	48.62
152.34	47.94
153.69	47.37
<u><math>C_{avg} = 151.59 \text{ nF}</math></u>	
<u><math>G_{avg} = 47.96 \text{ nF}</math></u>	

$$\nu = \frac{1}{2\pi} \sqrt{\frac{2}{LC}}$$

$$\nu_1 = \frac{1}{2\pi} \sqrt{\frac{2 \times 10^{12}}{0.981 \times 151.59}}$$

$$\boxed{\nu_1 = 18.46 \text{ kHz}}$$

$$\nu_2 = \frac{1}{2\pi} \sqrt{\frac{2}{LG}}$$

$$= \frac{1}{2\pi} \sqrt{\frac{2 \times 10^{12}}{0.981 \times 47.96}}$$

$$\boxed{\nu_2 = 32.81 \text{ kHz}}$$

## Inductance

$$\underline{L (\text{mH})}$$

0.992

0.980

0.982

0.984

0.974

0.983

0.986

0.972

0.973

0.986

$$\underline{L_{avg} = 0.981 \text{ mH}}$$

Calcu  
⑦

## Calculations :

### ① Monoatomic lattice

$$C_{avg} = 149.28 \text{ nF} \quad L_{avg} = 0.974 \text{ mH}$$

$$\text{From } \omega_{max} = \frac{1}{2\pi} \sqrt{\frac{1}{LC}} = 26.4 \text{ kHz.}$$

From the observations / plot,  $\omega_{max} = 27.05 \text{ kHz.}$

% deviation from theoretical value,

$$\begin{aligned} \% \text{ deviation} &= \left| \frac{(\omega_{max})_{exp.} - (\omega_{max})_{theo.}}{(\omega_{max})_{theo.}} \right| \times 100\% \\ &= \left| \frac{27.05 - 26.4}{26.4} \right| \times 100\% \end{aligned}$$

$$\underline{\% \text{ deviation} = 2.46\%}.$$

### ④ Monoatomic lattice $C_{avg} = 48.02 \text{ nF}$ $L_{avg} = 0.974 \text{ mH.}$

$$\text{From } \omega_{max} = \frac{1}{2\pi} \sqrt{\frac{1}{LC}} = 46.54 \text{ kHz.}$$

From observations / plots, we obtain  $\omega_{max} = 45.5 \text{ kHz.}$

% deviation from theoretical value,

$$\begin{aligned} \% \text{ deviation} &= \left| \frac{(\omega_{max})_{exp.} - (\omega_{max})_{theo.}}{(\omega_{max})_{theo.}} \right| \times 100\% \\ &= \left| \frac{45.5 - 46.54}{46.54} \right| \times 100\% \end{aligned}$$

$$\underline{\% \text{ deviations} = 2.23\%}.$$

(iii) Diatomic Lattice.

$$C_{avg} = 151.59 \text{ nF} \quad Q_{avg} = 47.96 \text{ nF}$$

$$L_{avg} = 0.181 \text{ mH}$$

From the formulae,

$$\nu_1 = \frac{1}{2\pi} \sqrt{\frac{2}{LC}}$$

$$\underline{\nu_1 = 18.46 \text{ kHz}}$$

$$\nu_2 = \frac{1}{2\pi} \sqrt{\frac{2}{LC}}$$

$$\underline{\nu_2 = 32.81 \text{ kHz}}$$

From the observations/plot, we obtain,

$$\underline{\nu_1_{obs.} = 19.55 \text{ kHz}}$$

$$\underline{\nu_2_{obs.} = 33.5 \text{ kHz.}}$$

$\therefore$  frequency band gap,  $\Delta\nu$ , theoretical,

$$\Delta\nu = (\nu_2 - \nu_1)_{theo.} = (32.81 - 18.46) \text{ kHz} \\ = \underline{14.35 \text{ kHz}}$$

experimental,  $\Delta\nu = (\nu_2 - \nu_1)_{exp.} = (33.5 - 19.55) \text{ kHz} \\ = \underline{13.95 \text{ kHz}}$

% deviation in band gap,  $= \frac{|(\Delta\nu)_{obs.} - (\Delta\nu)_{theo.}|}{(\Delta\nu)_{theo.}} \times 100\% \\ = \frac{|13.95 - 14.35|}{14.35} \times 100\%.$

% deviation in band gap = 2.79 %.

## Results & Discussion :-

- i) For a monoatomic lattice, phase difference per unit cell was measured for different frequencies using Lissajous figures &  $\gamma \propto \sqrt{s} \theta$  was plotted. The plot shows that as  $\theta$  increases,  $\gamma$  reaches a maximum (cut-off) frequency. The experiment was performed for two different capacitance circuits representing two different monatomic lattices with different masses.
- ii) Maximum frequency calculated, observed & % deviation is,  
for  $C_{avg} = 48.02\text{ nF}$ ,  $(\gamma_{max})_{calc.} = 46.54\text{ kHz}$   $(\gamma_{max})_{obs.} = 45.5\text{ kHz}$  &  
for  $C_{avg} = 149.29\text{ nF}$ ,  $(\gamma_{max})_{calc.} = 26.4\text{ kHz}$   $(\gamma_{max})_{obs.} = 27.05\text{ kHz}$   
with a % deviation of 2.23% & 2.45% respectively.
- iii) For a diatomic lattice, phase difference per unit cell was measured as a function of frequency. The dispersion curve shows two branches: lower frequency branch (acoustic) & a higher frequency branch (optical). The (frequency gap)/(band gap) was calculated & observed.  
 $(\Delta\gamma)_{calc.} = 14.35\text{ kHz}$   $(\Delta\gamma)_{obs.} = 13.75\text{ kHz}$ .  
with a % deviation of 2.79%.
- iii) The experiment demonstrates the analogy b/w mechanical lattice vibrations & electrical LC networks. Dispersion relation for both monoatomic & diatomic lattices were verified. Existence of cut-off frequency for monoatomic lattice & a band gap for diatomic lattice was observed.

## Results & Discussion :-

- i) For a monoatomic lattice, phase difference per unit cell was measured for different frequencies using Lissajous figures &  $\gamma \sqrt{3} \theta$  was plotted. The plot shows that as  $\theta$  increases, ~~it~~ reaches a maximum (cut-off) frequency. The experiment was performed for 2 different capacitance circuits representing two different monoatomic lattices with different masses.
- ii) Maximum frequency calculated, observed & % deviation is,  
for  $C_{avg} = 48.02 \text{ nF}$ ,  $(\gamma_{max})_{calc.} = 46.54 \text{ kHz}$   $(\gamma_{max})_{obs.} = 45.5 \text{ kHz}$  2%  
for  $C_{avg} = 149.29 \text{ nF}$ ,  $(\gamma_{max})_{calc.} = 26.4 \text{ kHz}$   $(\gamma_{max})_{obs.} = 27.05 \text{ kHz}$   
with a % deviation of 2.23 % & 2.45 % respectively.
- iii) For a diatomic lattice, phase difference per unit cell was measured as a function of frequency. The dispersion curve shows two branches: lower frequency branch (acoustic) & a higher frequency branch (optical). The band gap was calculated & observed.  
 $(\Delta\gamma)_{calc.} = 14.35 \text{ kHz}$   $(\Delta\gamma)_{obs.} = 13.95 \text{ kHz}$ .  
with a % deviation of 2.79 %.
- iii) The experiment demonstrates the analogy by mechanical relation for both monoatomic & diatomic lattices. Dispersion verified. Existence of cut-off frequency for monoatomic lattice & a band gap for diatomic lattice was observed.

viii) The experimental & theoretical values are within 3% deviation for all cases, hence the experiment matches reasonably with theoretical expectations. Minor deviations can be attributed to the following sources of errors.

### # Sources of Error :-

- i) Theoretical model assumes an infinite lattice, however we worked with 5-10 unit cells in the electrical analog.
- ii) Internal resistance of inductors can cause damping in oscillations & alter the measurements.
- iii) Heating of components can alter the values of capacitances & inductances, affecting the measurements.

